

Technician Exam 2018-2021 - Questions on Ohm's Law and Power (T5C and T5D) – Chapter 3

T5C09 — How much power is being used in a circuit when the applied voltage is 13.8 volts and the current is 10 amperes?

Power equals Voltage multiplied by Current

$$P = E \times I = 13.8 \text{ V} \times 10 \text{ A} = 138 \text{ W}$$

T5C10 — How much power is being used in a circuit when the applied voltage is 12 volts DC and the current is 2.5 amperes?

Power equals Voltage multiplied by Current

$$P = E \times I = 12 \text{ V} \times 2.5 \text{ A} = 30 \text{ W}$$

T5C11 — How many amperes are flowing in a circuit when the applied voltage is 12 volts and the load is 120 watts?

Current equals Power divided by Voltage

$$I = P / E = 240 \text{ W} / 12 \text{ V} = 20 \text{ A}$$

(Practice only) What is the voltage in a circuit if a 50-watt load draws 5 amps?

Power equals Voltage multiplied by Current

$$E = P / I = 50 \text{ W} / 5 \text{ A} = 10 \text{ V}$$

T5D04 — What is the resistance of a circuit in which a current of 3 amperes flows through a resistor connected to 90 volts?

Resistance equals Voltage divided by Current

$$R = E / I = 90 \text{ V} / 3 \text{ A} = 30 \Omega$$

T5D05 — What is the resistance in a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

Resistance equals Voltage divided by Current

$$R = E / I = 12 \text{ V} / 1.5 \text{ A} = 8 \Omega$$

T5D06 — What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

Resistance equals Voltage divided by Current

$$R = E / I = 12 \text{ V} / 4 \text{ A} = 3 \text{ W}$$

T5D07 — What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

Current equals Voltage divided by Resistance

$$I = E / R = 120 \text{ V} / 80 \text{ } \Omega = 1.5 \text{ A}$$

T5D08 — What is the current through a 100-ohm resistor connected across 200 volts?

Current equals Voltage divided by Resistance

$$I = E / R = 200 \text{ V} / 100 \text{ } \Omega = 2 \text{ A}$$

T5D09 — What is the current through a 24-ohm resistor connected across 240 volts?

Current equals Voltage divided by Resistance

$$I = E / R = 240 \text{ V} / 24 \text{ } \Omega = 10 \text{ A}$$

T5D10 — What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

Voltage equals Current multiplied by Resistance

$$E = I \times R = 0.5 \text{ A} \times 2 \text{ } \Omega = 1 \text{ V}$$

T5D11 — What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

Voltage equals Current multiplied by Resistance

$$E = I \times R = 1 \text{ A} \times 10 \text{ } \Omega = 10 \text{ V}$$

T5D12 — What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

Voltage equals Current multiplied by Resistance

$$E = I \times R = 2 \text{ A} \times 10 \text{ } \Omega = 20 \text{ V}$$